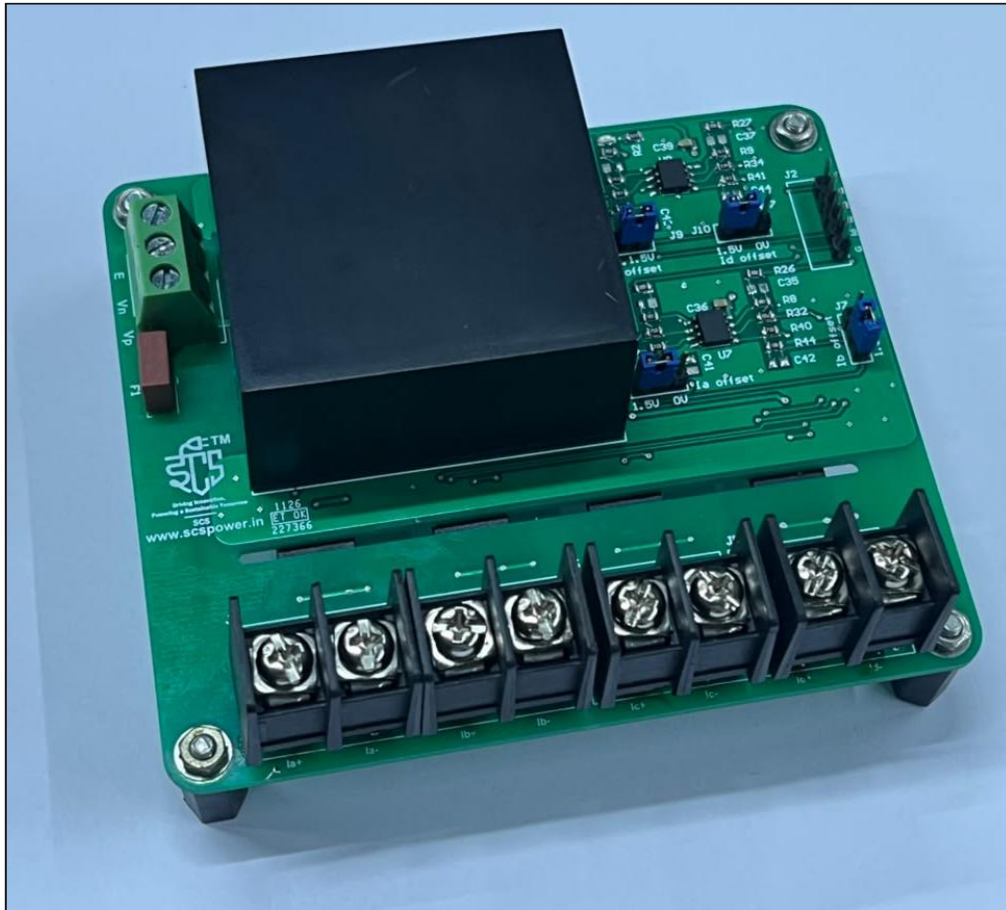




## User Manual

# SCS04HFCSXXX

## (High Frequency Current Sensors Board)



Prepared By: SCS

[www.scspower.in](http://www.scspower.in) [info@scspower.in](mailto:info@scspower.in)

Smart Charging Solutions (SCS) reserves the copyright and right of final interpretation. Other trademarks, products, and company names are the property of their respective owners and do not imply specific product and/or vendor endorsement, sponsorship, or association.  
Jan, 2025. Rev. – 1.1



---

## Overview:

- AC/DC universal current sensors board.
- On board auxiliary power supplies.
- Excellent accuracy and linearity.
- Thermal and noise optimized PCB design.
- Up to four onboard current sensors.
- Current sensing bandwidth >250 kHz.
- Current sensing range maximum up to 50 A.
- Selectable offset 0V and 1.5V.
- Current sensing accuracy better than  $\pm 1\%$
- Board can be power up with single phase 85-300Vac power supply.
- LED indication for power on.

## Board Protection:

- Over Current
- Over Voltage
- Short Circuit
- As per IEC 61000-4 Standard

## Applications:

This board is universal and can be used for any application whether AC or DC current sensing and have frequency bandwidth of 250kHz, some of the targeted applications are,

- Power Converters
- Electrical Drives
- General purpose industry applications
- Laboratory R&D purposes
- Testing purposes



Table 1 Pinout

Number	Name	Description
1.	$V_p$	Positive terminal for AC voltage supply
2.	$V_n$	Negative terminal for AC voltage supply
3.	E	Earth terminal
4.	$I_{a+}, I_{b+}, I_{c+}, I_{d+}, I_{a-}, I_{b-}, I_{c-}, I_{d-}$	terminals for the sensing current input
5.	$I_a, I_b, I_c, I_d$	Sensor output
6.	G	Ground terminal

## Offset setting

Each 3-pin header (J15, J16, J17, J18) in the sensing circuit is provided for selecting the required Offset:

- 0V: Install the jumper between the 0V pins.
- 1.5V: Install the jumper between the 1.5V pins.

Table 2 Sensor Offset Jumper pin Identification

Sr. No.	Indicator	Description
1	J15	For A Current sensor
2	J16	For C Current sensor
3	J17	For B Current sensor
4	J18	For D Current sensor

## 2 Sensor Gain Calculation

### 2.1 Conversion Formulas

$$\text{Gain} = \frac{I_{IN}}{V_{OUT}}$$

Take three different readings and then average for better accuracy. For better calculation of gain use sensor near to its rated Current values.

Use accurate multi-meter for calibrate sensors, use AC range for AC measurements.

To obtain original wave shape in microcontroller/DSP/FPGA/DSPACE:

The current outputs are available in voltage form on pins  $I_a, I_b, I_c, I_d$ , all referenced to GND. Each output pin has a fixed gain. In the microcontroller, simply multiply the ADC value by the gain in non-offset mode, and in offset mode, subtract 1.5 V from the ADC value first and then apply the gain.



**Table 3 Sample AC Current Gain Calculation At  $I_a$**

Input rms current(A)	Output rms voltage(V)	Gain
4.82	0.489	9.856
3.87	0.392	9.872
2.94	0.295	9.966
2.07	0.205	10.09
1.20	0.115	10.43
	<b>Average Gain</b>	10.04

## 2.2 Gain Calculation Examples

### Example 1

Given:

- Input rms Current ( $I_{in}$ ): 3.87 A
- Measured Output rms Voltage ( $V_{out}$ ): 0.392 V

Gain:

$$\text{Gain} = \frac{I_{IN}}{V_{OUT}}$$

$$\text{Gain} = \frac{3.87}{0.392} = 9.872$$



## 3. Experimental Validation

### 3.1 Setup

A SIGLENT SDS824 oscilloscope and FLUKE 15B+ Digital multimeter was used to monitor the output voltage and input current. The overall experimental setup is shown below.

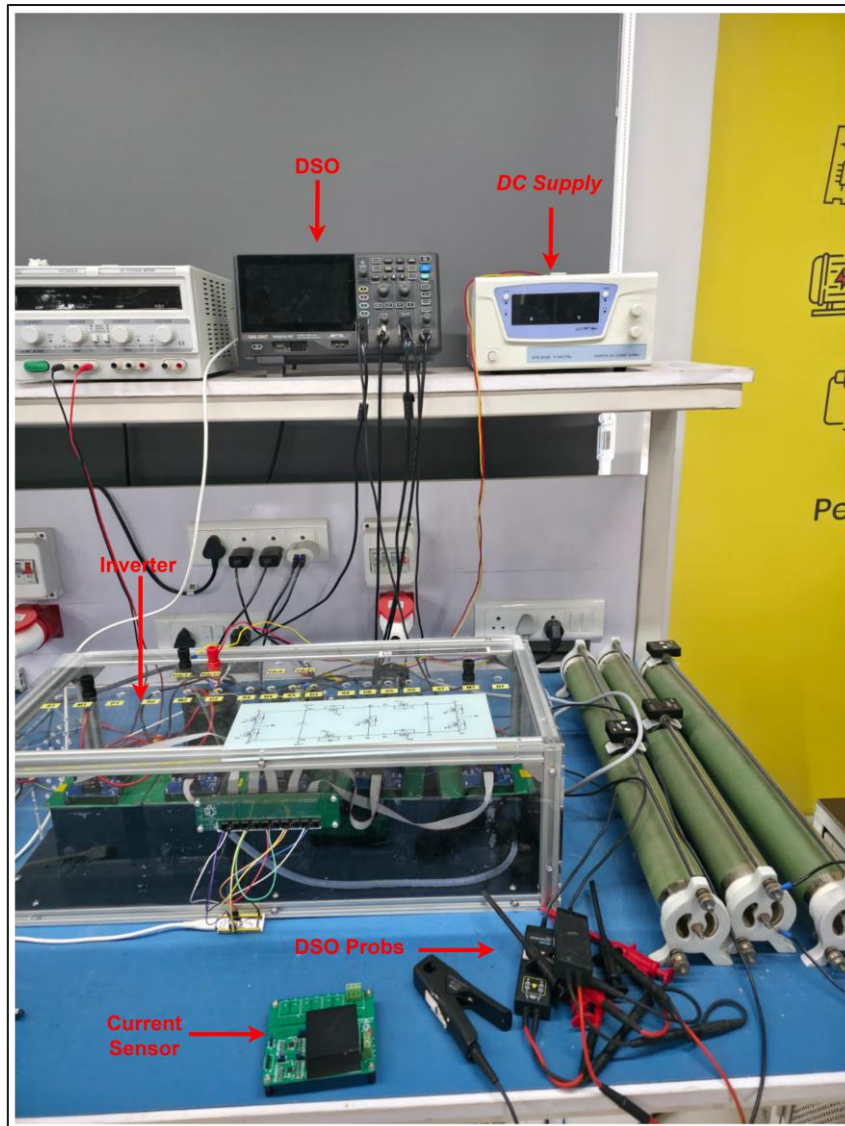


Figure 1 : Experimental setup



### 3.2 Experimental Results

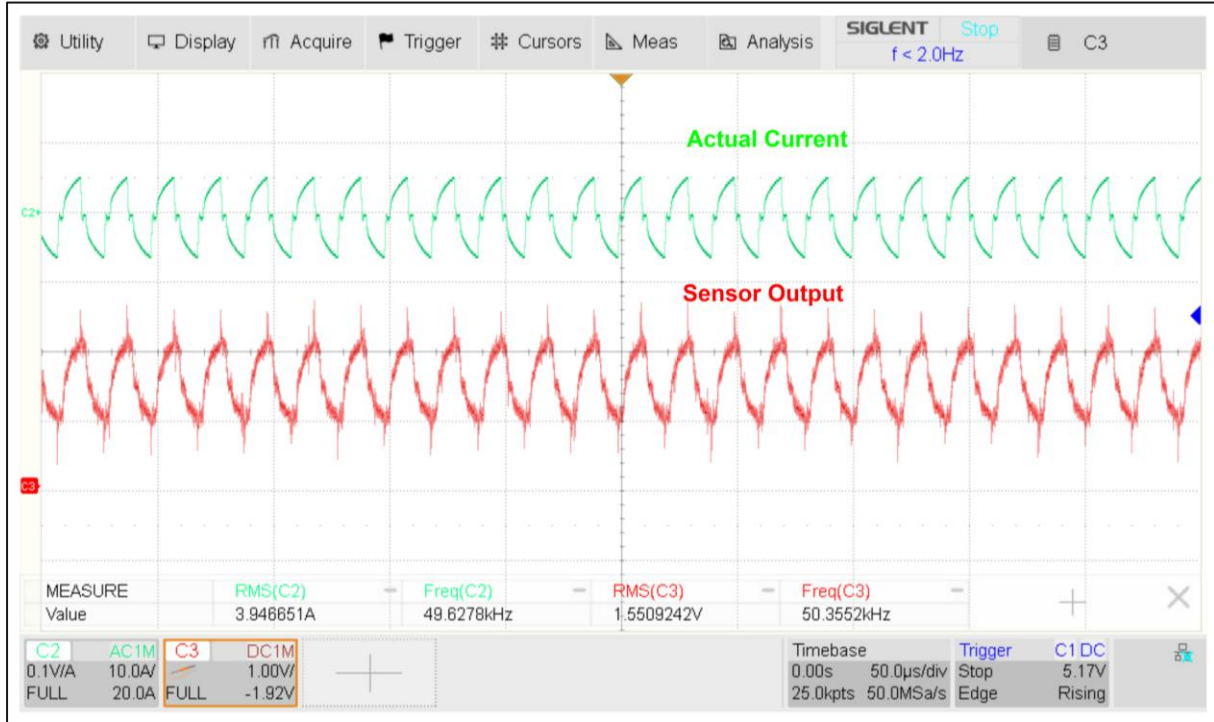


Figure 2 : Results with 50kHz current